

Level : B. E./B.Sc.
Year : II

Course : EEG 211
Semester: I

Exam Roll No. :

Time: 30 mins.

F. M. : 20

Registration No.:

Date 07 JUN 2019

SECTION "A"

[20 Q × 1 = 20 marks]

Choose the most appropriate answer. Symbols have their usual meaning.

1. Circuit shown in Figure 1 is _____.
- [a] small signal model of an amplifier [b] large signal model of an amplifier
[c] small signal model of a diode [d] large signal model of a diode.

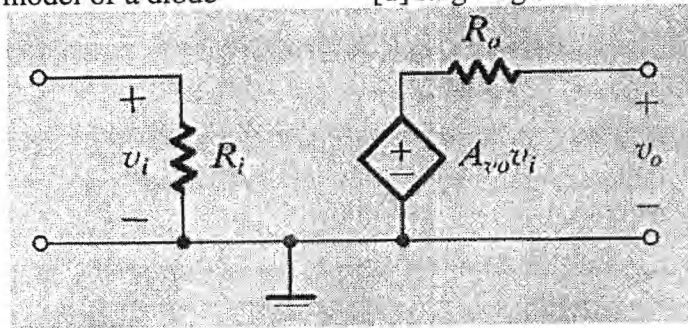


Figure: 1

2. Voltage gain of an amplifier _____.
- [a] must be less than 1 [b] must be very large
[c] must be negative [d] is dimensionless
3. Frequency response curve of an amplifier shows variation of _____.
- [a] voltage with frequency [b] time with frequency
[c] phase with frequency [d] current gain with frequency
4. dBm is a unit used to express _____.
- [a] voltage gain [b] current gain [c] volatge [d] power
5. Analog signal rectification is normally done by using _____.
- [a] a resistor [b] a capacitor
[c] a diode [d] a transistor
6. Two diodes connected in series can be considered as _____.
- [a] a battery of 1.4 volts [b] a current source of 0.7 A
[c] a battery of 2.8 volts [d] a current source of 2.8 A
7. Bipolar Junction Transistor has _____ junctions.
- [a] 5 [b] 4 [c] 3 [d] 2
8. The relation, $I_C = \beta I_B$ is valid for a transistor operating in _____ region.
- [a] saturation [b] cut-off [c] active [d] triode

9. A Bipolar Junction Transistor operating in the active region has maximum _____.
 [a] base current [b] emitter current [c] collector current [d] gate current
10. g_m of a Bipolar Junction Transistor relates _____.
 [a] collector current with collector potential
 [b] emitter current with emitter potential
 [c] collector current with emitter to base potential difference
 [d] base current with collector to base potential difference
11. If V_{CE} in the circuit of Figure 2 is V_{CC} , the transistor is working in the _____ region.
 [a] active [b] cut-off [c] triode [d] saturation

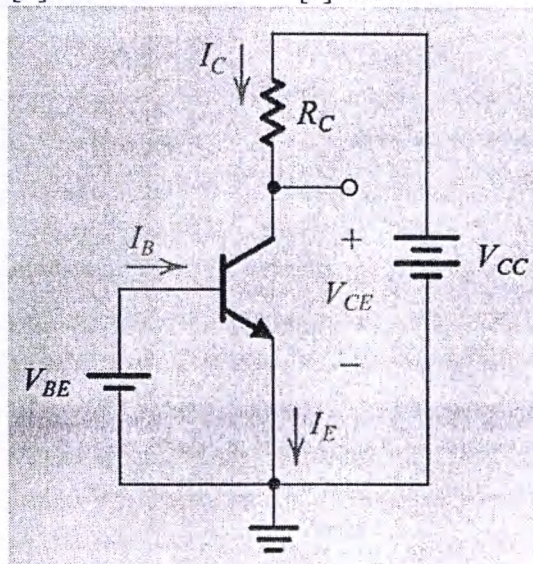


Figure: 2

12. In a NMOS Field Effect Transistor operating in the active region, overdrive voltage is _____.
 [a] $V_{GS} + V_t$ [b] $V_{GS} - V_t$ [c] $V_{SG} + V_t$ [d] $V_{SG} - V_t$
13. In the circuit of Figure 3, the transistor will operate in the _____ region.
 [a] cut-off [b] saturation [c] triode [d] deep triode


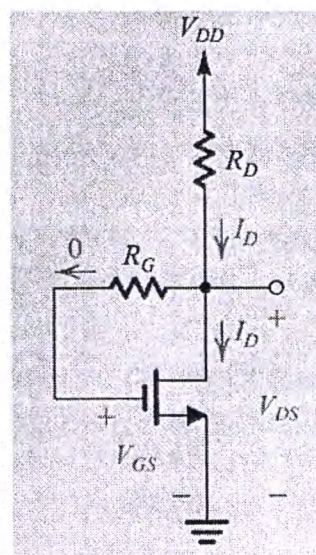


Figure: 3

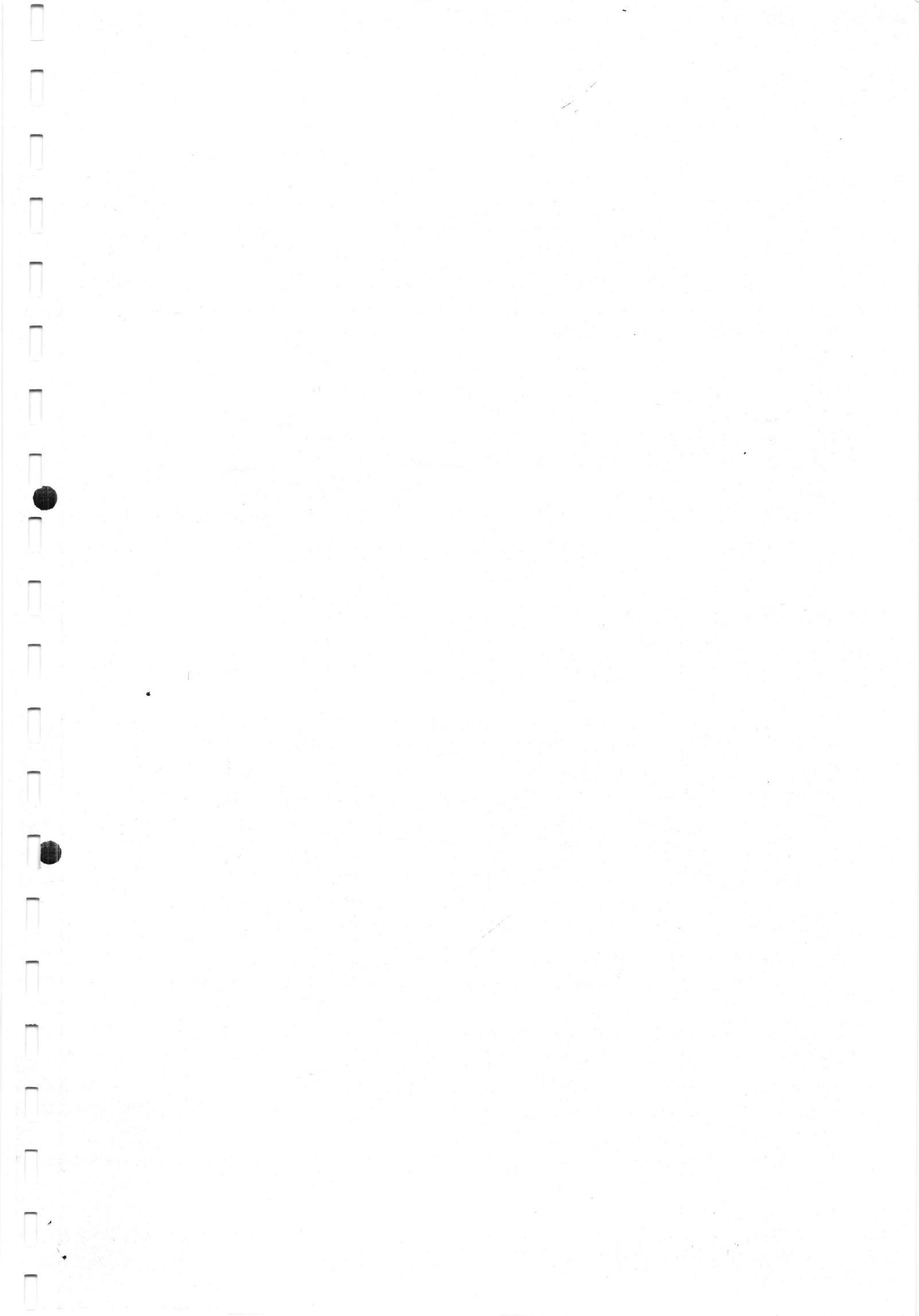14. The input impedance of a MOS Field Effect Transistor is _____.
[a] 0Ω [b] $1 \text{ M}\Omega$
[c] ∞ [d] bias current dependent
15. Typical class B amplifiers have _____ transistor/s.
[a] 1 [b] 2 [c] 3 [d] 4
16. _____ amplifier needs biasing.
[a] class A [b] class B [c] class C [d] class D
17. The maximum efficiency of a class A structure is _____%.
[a] 25 [b] 60 [c] 78 [d] 80
18. Operational amplifier amplifies _____.
[a] ratio of two input signals [b] product of two input signals
[c] sum of two input signals [d] difference of two input signals
19. If two inputs of a differential amplifier are equal, the output voltage _____.
[a] becomes zero [b] reaches maximum
[c] reaches minimum [d] saturates
20. In a typical differential amplifier structure, there are _____ transistors.
[a] 5 [b] 4 [c] 3 [d] 2



Level : B. E./B.Sc.
Year : II
Time : 2 hrs. 30 mins.

SECTION "B"

[5Q. \times 11 = 55 marks]

Attempt *ANY FIVE* questions.
Assume suitable data where necessary.
All Symbols have their usual meanings.

1.
 - a. Derive an expression for small signal resistance of a diode when it is forward biased by I_D current at room temperature. [5]
 - b. Draw and explain the peak of the peaks detector circuit. [6]
2.
 - a. With figure, explain cut-off region, active region, and saturation region of a Bipolar Junction Transistor. [5]
 - b. Show that the transistor of Figure 1 is working in the saturation region. [6]

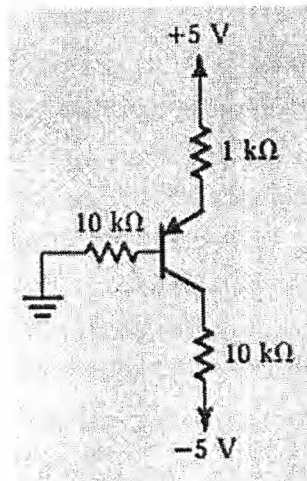


Figure: 1

3.
 - a. The NMOS in the circuit of Figure 2 has threshold voltage of 1V, $k_n'(W/L) = 1 \text{ mA/V}^2$, and $V_D = 0.1 \text{ V}$. Find the value of R_D . [5]

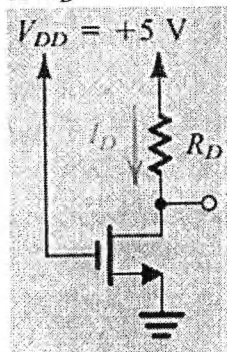


Figure: 2

- b. With explanation, draw drain current (i_D) versus gate to source potential difference (v_{GS}) and drain current (i_D) versus drain to source potential difference (v_{DS}) for a NMOS type Field Effect Transistor operating in the active region. [6]
- 4.
- a. Draw the small signal equivalent circuit of a NMOS Field Effect Transistor and NPN Bipolar Junction Transistor. [5]
- b. What is frequency response of an amplifier? In the frequency response curve, show the upper and lower 3 dB frequencies. [6]
- 5.
- a. Draw typical circuit of class A and class B amplifiers. What is cross over distortion in class B amplifier? [5]
- b. Derive an expression for efficiency of a class A amplifier. Also find maximum efficiency that can be achieved by class A amplifier? [6]
- 6.
- a. Draw a circuit of a differential amplifier and explain its working. Use Bipolar Junction Transistor for the design. [5]
- b. For the operational amplifier circuit in Figure 3, find the current through R_1 , current through R_2 , and the output voltage (v_O) in terms of input voltage (v_I). [6]

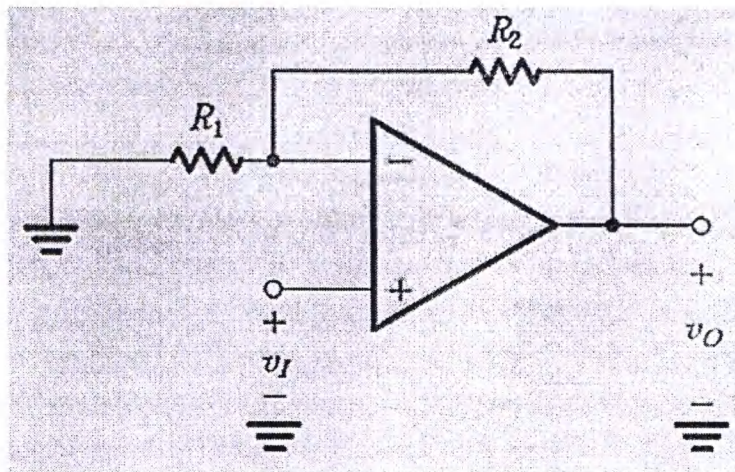


Figure: 3